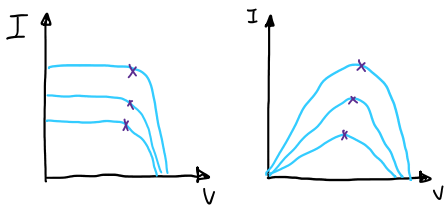




# MPPT: DC-DC

Tuesday, March 5, 2024 4:00 PM
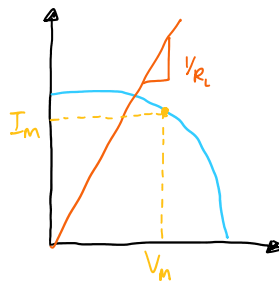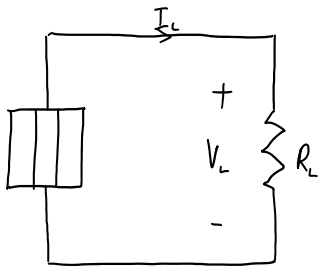
## Maximum Power Point Tracking




As ambient conditions change, the optimal operating point  $(V, I)$  moves around



In general,  
 $(V_L, I_L) \neq (V_{mpp}, I_{mpp})$

• GOAL Design a circuit to track the MPP

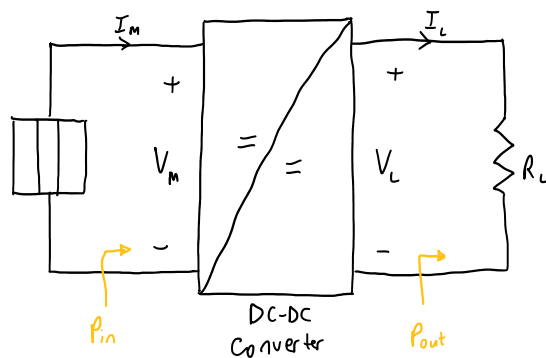


Desired characteristics:

- 1)  $\eta = 100\%$  or  $V_m I_m = V_L I_L$
- 2) Control capability as MPP changes, want to fix operation at MPP

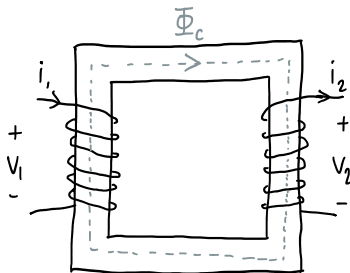• QUESTION How to construct DC-DC converter?

• Seek inspiration from AC domain  $\rightarrow$  transformers



Faraday's Law:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}, \quad N_1 i_1 = N_2 i_2$$

Ideal transformer:  $V_1 i_1 = V_2 i_2$

$\rightarrow$  transformer saturates at DC

→ turns ratio is fixed, but we want increased flexibility/control


- DC-DC converters

- buck converter
- boost converter
- buck-boost converter
- flyback, Cuk, etc. ...

- Composed of energy storage (C, L), switches (FETs, diodes), control (digital, analog)

- Some fundamentals

1)

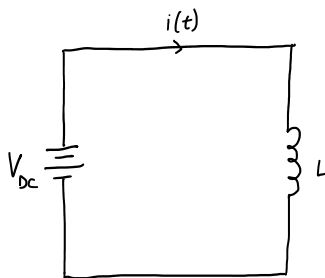


$$V_{dc} = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_{dc}}{L}$$

→  $i(t) \uparrow$

BAD IDEA

2)

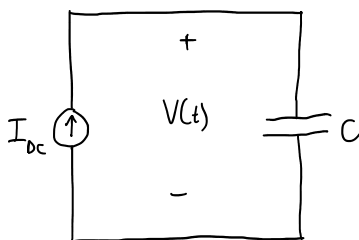

$$I_{dc} = C \frac{dV}{dt}$$

→  $V(t) \uparrow$  by similar logic from ①


BAD IDEA

- Relevant because DC-DC converters are composed of L and C.

- Guiding principle

- $\langle V_L \rangle = 0$
- $\langle i_C \rangle = 0$

### 3) Switching Waveform

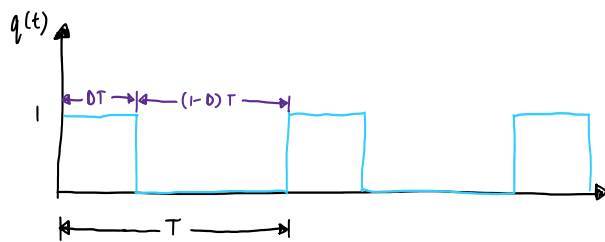


$$\langle q(t) \rangle = \frac{1 \times DT + 0 \times (1-D)T}{T}$$

$$= D \quad 0 \leq D \leq 1$$

↑  
duty cycle

- DC-DC converters have switches that are controlled by "switching signals"
- Average behaviour is important in DC-DC converters


### • DC-DC Buck Converter

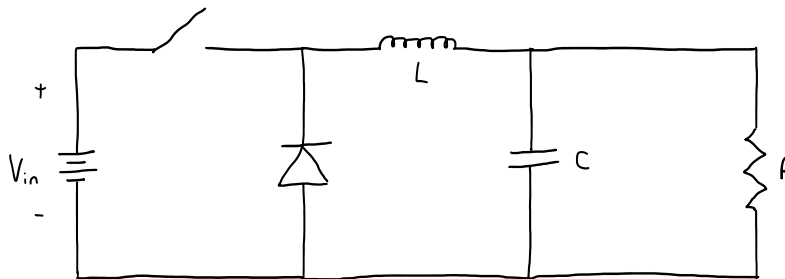

- Ideal switch controlled by  $q(t)$
- Ideal diode
- Energy Storage  $L, C$


### • Operating Principle

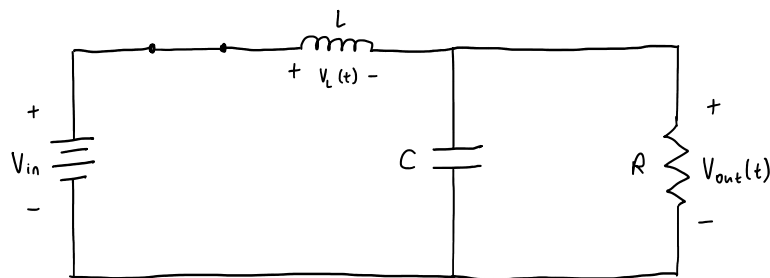1) When switch is closed, diode is in reverse bias



$$V_L(t) = V_{in} - V_{out}(t)$$

2) When switch is open.

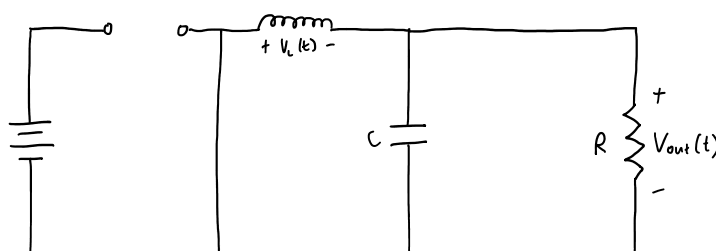

$$V_L(t) = -V_{out}(t)$$

- If capacitor is large,  $V_{out} \approx \text{constant} = V_{out}$

on average


$$\langle V_L(t) \rangle = 0 = \frac{1}{T} (DT(V_{in} - V_{out}) + (1-D)T(-V_{out}))$$

$$0 = DV_{in} - DV_{out} - V_{out} + DV_{out}$$

$$\boxed{V_{out} = DV_{in}} \quad 0 \leq D \leq 1$$

- Since  $D$  is tunable, we have built a controllable DC-DC converter that can deliver output voltage  $<$  input voltage

- Wave forms

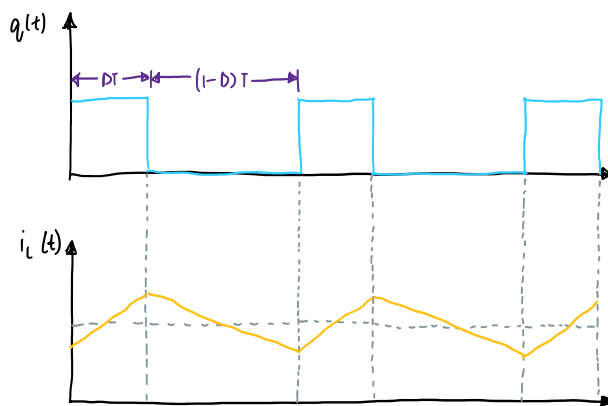

Large  $C \rightarrow$  effectively DC voltage source with some small ripple


Large  $L \rightarrow$  effectively DC current source with some small ripple

1) Switch closed:  $V_L(t) = V_{in} - V_{out} = 0$   
 $\frac{di_L}{dt} > 0 \rightarrow i_L(t) \uparrow$


2) Switch open:  $V_L(t) = -V_{out}$   
 $\frac{di_L}{dt} < 0 \rightarrow i_L(t) \downarrow$

- What if we want  $V_{out} > V_{in}$ ?  $\rightarrow$  Boost Converter

# • DC-DC Boost Converter

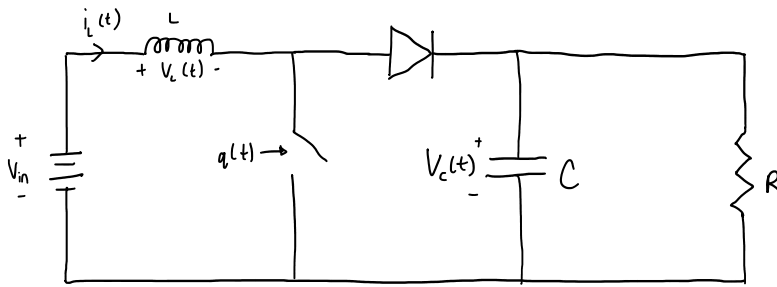


• Switch is open, diode in full bias

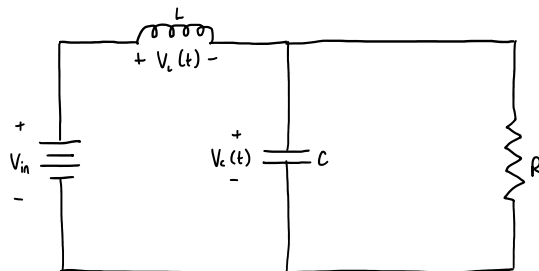

$$V_L(t) = V_{in} - V_{out}(t)$$

• Switch is closed

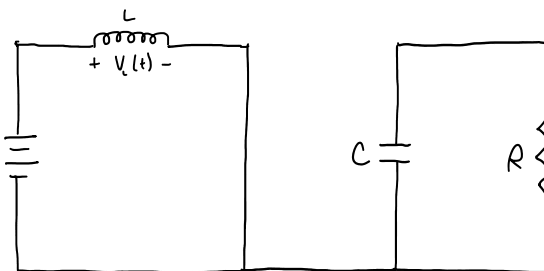

$$V_L(t) = V_{in} \rightarrow i_L(t) \uparrow$$

$$V_L(t) = q(t) V_{in} + (1 - q(t))(V_{in} - V_{out}(t))$$

$$C \text{ is large} \rightarrow V_{out}(t) \approx V_{out} \text{ constant}$$

$$\langle V_L(t) \rangle = 0 = \langle q(t) \rangle V_{in} + \langle 1 - q(t) \rangle (V_{in} - V_{out})$$

$$= D V_{in} + (1 - D)(V_{in} - V_{out})$$


$$= D V_{in} + V_{in} - V_{out} - D V_{in} + D V_{out}$$

$$= V_{in} - (1 - D) V_{out}$$

$$V_{out} = \frac{1}{1 - D} V_{in}$$

$$\frac{V_{out}}{V_{in}} \uparrow$$

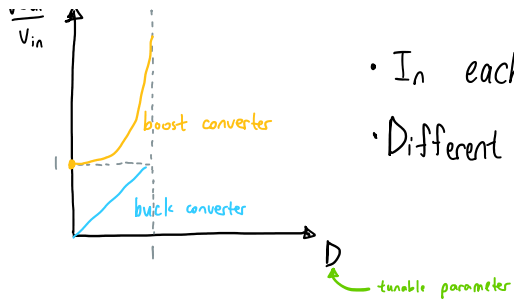• In each topology, we have  $V_{out} = f(D) V_{in}$



- In each topology, we have  $V_{out} = f(D) V_{in}$
- Different  $f(D)$  can result in  $V_{out} \leq V_{in}$  (buck),  $V_{out} \geq V_{in}$  (boost), or either (buck-boost)