
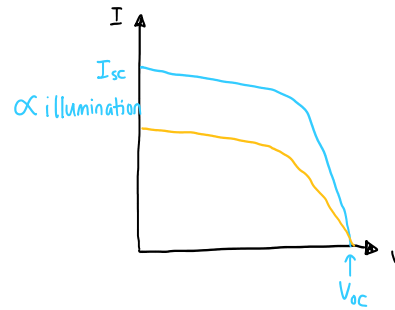


Max Power Point

Tuesday, February 27, 2024

4:00 PM

Equivalent Circuit Model for PV cell

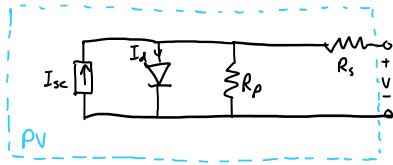


$$I = I_{sc} - I_0 \left(e^{\frac{qV_d}{kT}} - 1 \right) - \frac{V_d}{R_p}$$


$$V_d = V + IR_s$$

Cells \rightarrow Modules \rightarrow Arrays

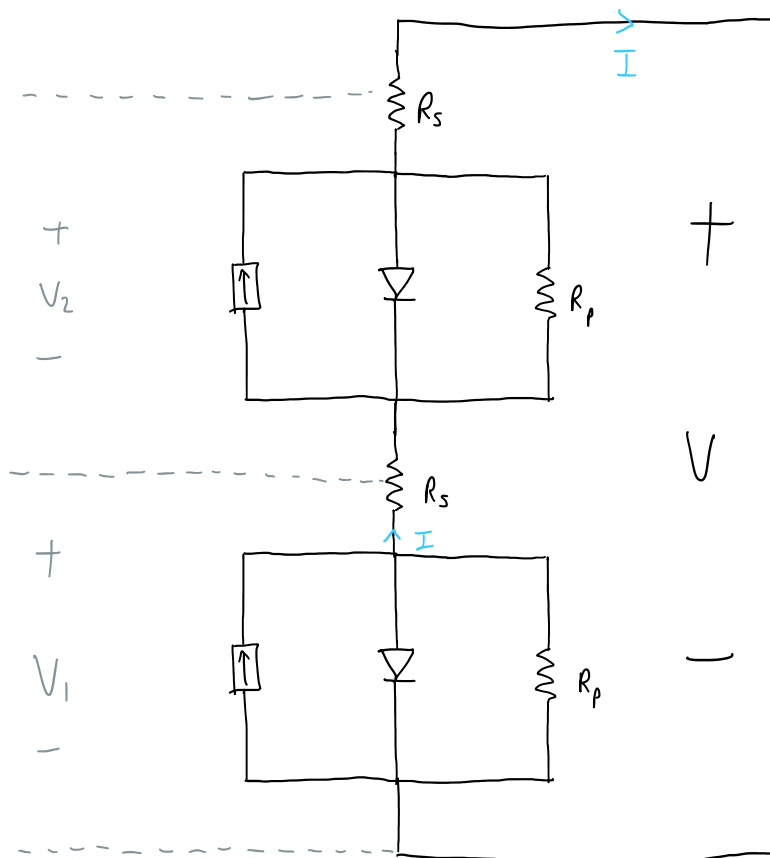- individual cells only produce $\sim 0.5V$ at output
 - > want to connect them in series
 - > may also want to connect in parallel for more current


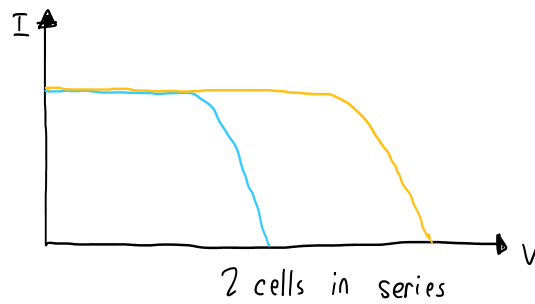
$$\begin{aligned} V &= V_1 + V_2 \\ &= (V_d - IR_s) + (V_d - IR_s) \\ &= 2(V_d - IR_s) \end{aligned}$$



In general, for n cells in series:

$$V = n(V_d - IR_s)$$

Modules — cells in series. 36, 72, 96, ...

• Ex 72 identical cells connected in series, 1 sun insolation (1 kW/m^2)

For each cell, $I_{sc} = 6 \text{ A}$ @ 25°C , $I_0 = 5 \times 10^{-11} \text{ A}$, $R_p = 10 \Omega$, $R_s = 0.001 \Omega$,

$V_d = 0.57 \text{ V}$.


$$\begin{aligned} I &= I_{sc} - I_0 \left(e^{\frac{38.9 V_d}{V_d}} - 1 \right) - \frac{V_d}{10} \\ &= 6 - (5 \times 10^{-11}) (e^{(38.9)(0.57)} - 1) - \frac{0.57}{10} \\ &= 5.73 \text{ A} \end{aligned}$$


$$\begin{aligned} V_{\text{module}} &= n(V_d - IR_s) \\ &= 72(0.57 - 5.73 \times 0.001) \\ &= 40.6 \text{ V} \end{aligned}$$

$$\begin{aligned} P &= V_{\text{module}} I \\ &= (40.6)(5.73) \\ &= 233 \text{ W} \end{aligned}$$


• Arrays

• connect modules in series or parallel

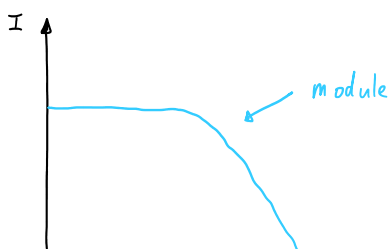


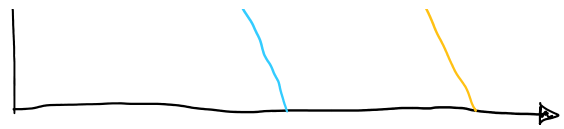




Parallel

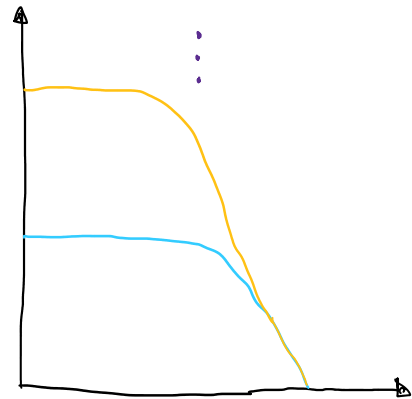

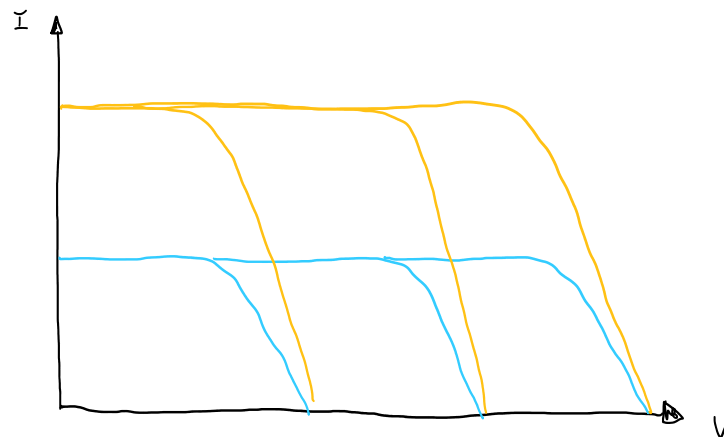- What about parallel combination of 3 series-connected modules?




Maximum Power Tracking

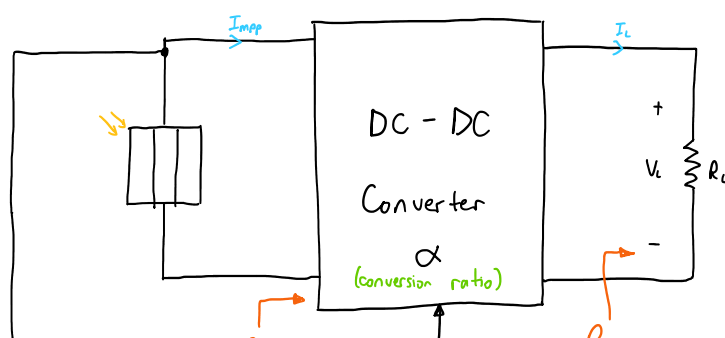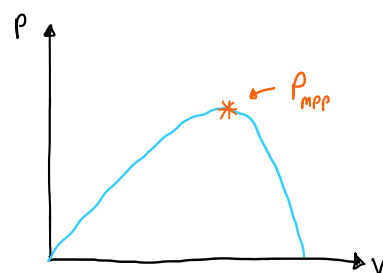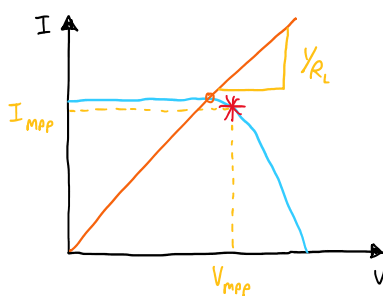

Ideally:

$$V_L = \alpha V_{mpp}$$

$$I_L = \frac{1}{\alpha} I_{mpp}$$

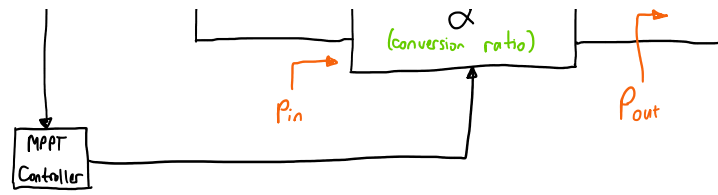

$$P_L = \alpha \cdot P_{MPP}$$