



Shading+Bypass

Thursday, February 29, 2024

3:43 PM

MT coverage until this lecture, up to HW3


PV cell equivalent model

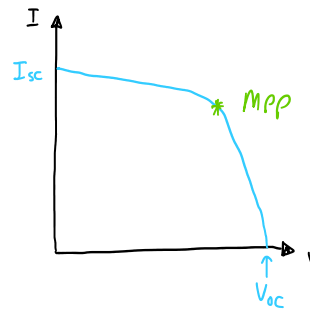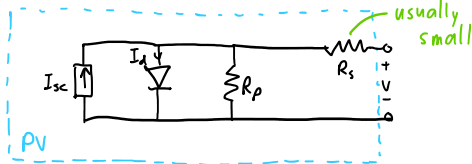

PV cells $\xrightarrow{\text{series}}$ module $\xrightarrow{\text{series/parallel}}$ array

Shading Impacts on I-V Curves

- Consider n cells in series

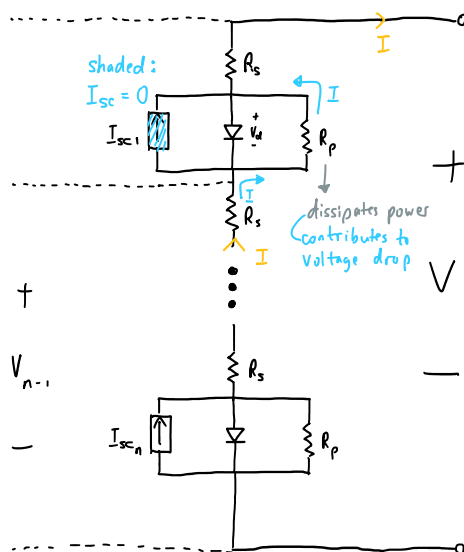

Suppose $I_{sc1} = I_{sc2} = \dots = I_{scn}$. Then,

$$V = n (V_d - I R_s) \rightarrow V_d = \frac{V}{n} + I R_s. \text{ Also,}$$

$$I = I_{sc} - I_d - \frac{V_d}{R_p} \rightarrow I = I_{sc} - I_0 \left(e^{\frac{qV_d}{kT}} - 1 \right) - \frac{V_d}{R_p}$$

$$= I_{sc} - I_0 \left(e^{q \left(\frac{V}{n} + I R_s \right) / (kT)} - 1 \right) - \frac{\frac{V}{n} + I R_s}{R_p}$$

In practice, $I_{sc1} \neq I_{sc2} \neq \dots \neq I_{scn}$.

- Consider extreme case of $I_{sc1} = 0$ (total shading of 1 cell)
 - Diode is reverse bias
 - I goes through R_p and R_s
 - Shaded cell acts as a resistive load!
 - Causes voltage drop across shaded cells

- Causes voltage drop across shaded cells

$$V_{SH} = V_{n-1} - I(R_p + R_s)$$


$$V_{n-1} = \left(\frac{n-1}{n}\right)V$$

$$V_{SH} = \frac{n-1}{n} V - I(R_p + R_s)$$

$$\Delta V = V - V_{SH} = V - \left(\frac{n-1}{n}\right)V + I(R_p + R_s)$$

$$= V - \left(1 - \frac{1}{n}\right)V + I(R_p + R_s)$$
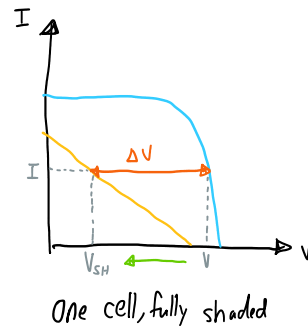
$$= V - V + \frac{1}{n}V + I(R_p + R_s)$$



$$\Delta V \approx \frac{1}{n}V + IR_p \quad \text{because } R_s \ll R_p$$

• Example


- 72 identical cells in a module, wired in series
- 1-sun insolation (1 kW/m^2)

- Hot Spot


- Power dissipated as heat can cause a local hot spot
- May permanently damage plastic laminates enclosing the cell

Bypass Diodes

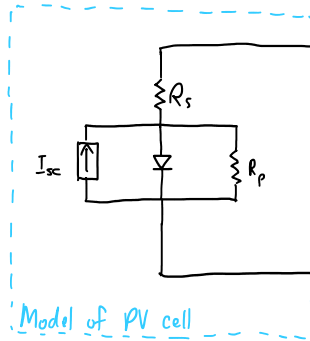
- Shaded cell contributes to voltage drop
 - consumes/dissipates instead of generates power ☹️
- IDEA💡: limit amount of voltage drop by adding a bypass diode



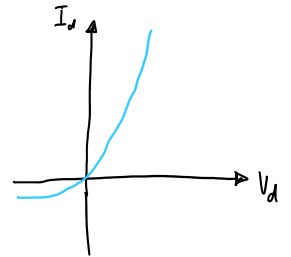Path of least resistance diode in forward bias
Contributes to $\sim 0.5V$ voltage drop (compared to $17V$
in example before)



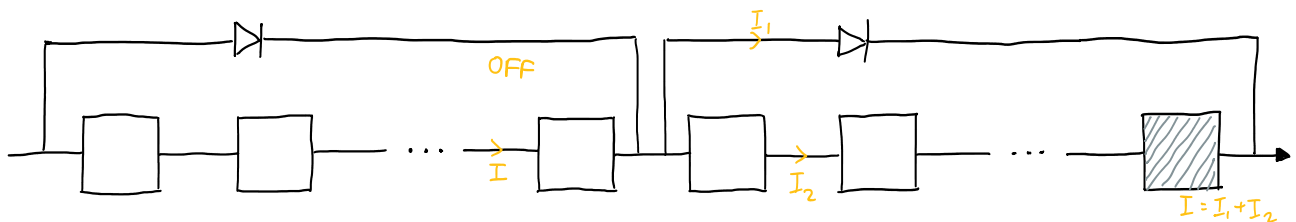- IDEAL: Put a bypass diode across every cell
- REALITY: Typically connected across every 18-24 cells, 3-4 bypass diodes in 72-cell string



~~~~~ END OF MT COVERAGE ~~~~~