
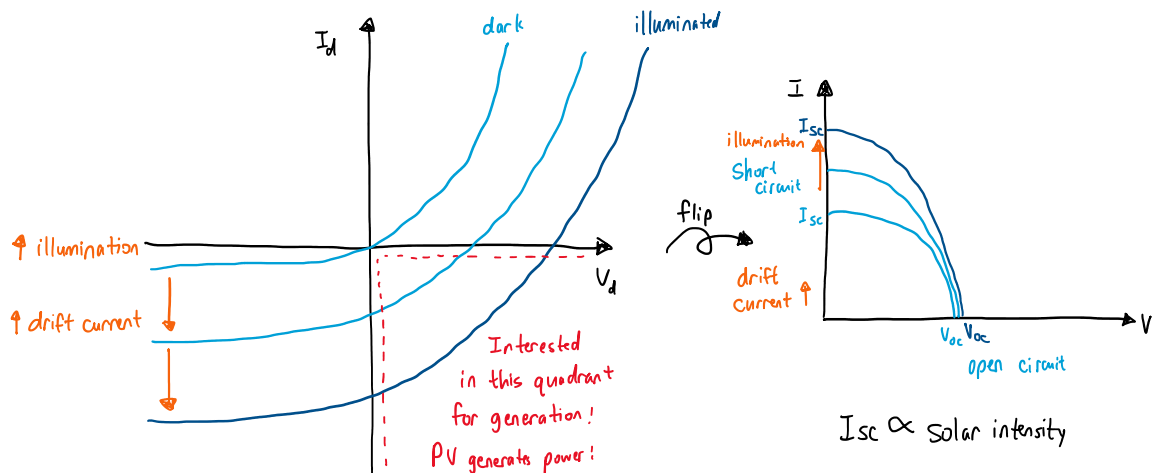


PN Junction Circuit

Thursday, February 15, 2024 3:59 PM

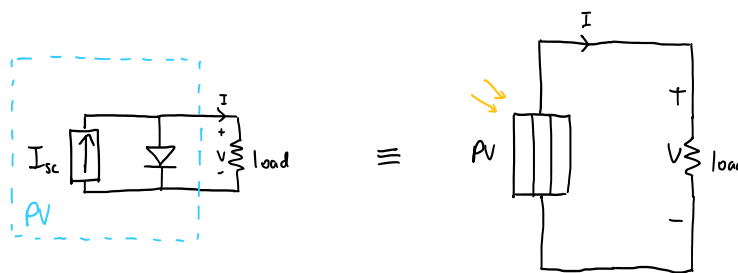


- A useful circuit to describe this behaviour




- From this model, $I = I_{sc} - I_d = I_{sc} - I_0(e^{\frac{qV_d}{kT}} - 1)$ at 25°C (often used as standard).

$$I_d = I_0(e^{38.9V} - 1)$$

- 2 important characteristics of PV cell

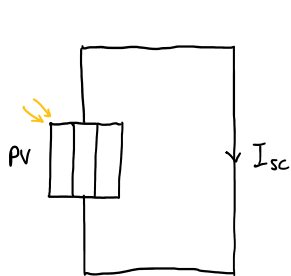

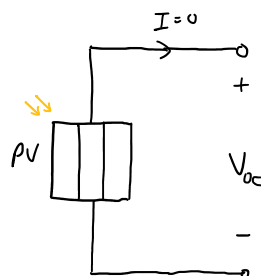Short-circuit current
set $V=0$, $I = I_{sc}$



Open-circuit voltage

$$\begin{aligned} \text{set } I &= 0 \\ \frac{I_{sc}}{I_0} &= e^{\frac{qV_{oc}}{kT}} - 1 \\ \frac{qV_{oc}}{kT} &= \ln\left(\frac{I_{sc}}{I_0} + 1\right) \\ V_{oc} &= \frac{kT}{q} \ln\left(\frac{I_{sc}}{I_0} + 1\right) \end{aligned}$$

- Ex. 150 cm^2 PV cell with reverse saturation current $I_0 = 10^{-12} \text{ A/cm}^2$. In "full sun" (1 kW/m^2), it produces short-circuit current of 40 mA/cm^2 at 25°C . What is I_{sc} , V_{oc} ?


$$I_{sc} = 0.04 \times 150 = 6 \text{ A}$$

$$V_{sc} = \frac{kT}{q} \ln\left(\frac{I_{sc}}{I_0} + 1\right) = 0.0257 \ln\left(\frac{6}{10^{-12} \times 150} + 1\right) = 0.627 \text{ V}$$


What about for "half sun?"

$$I_{sc} = 3 \text{ A}$$

$$V_{sc} = 0.610 \text{ V}$$

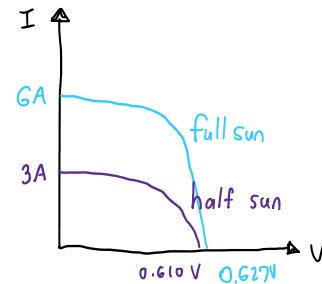


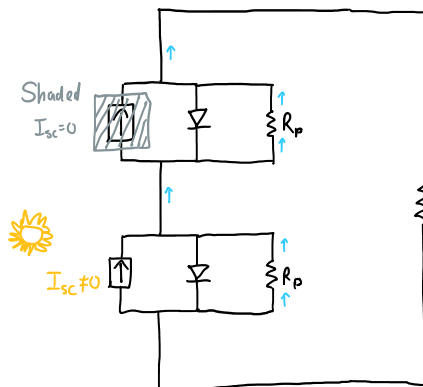- More accurate circuit models of PV cell




- For meaningful output voltage, connect PV cells in series
- In reality, there is current that goes to load
→ Add leakage resistance in parallel
- This way, current can pass through the shaded cell

- Updated circuit model

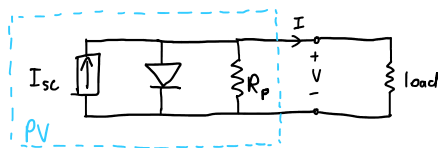


$$I = I_{sc} - I_d - \frac{V}{R_p}$$

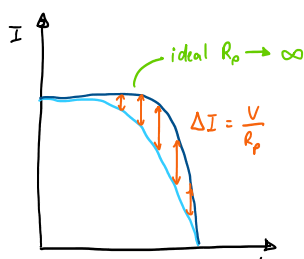- typically, in this model R_p is large.
- allows small amount of current to pass



_____ \vec{v}

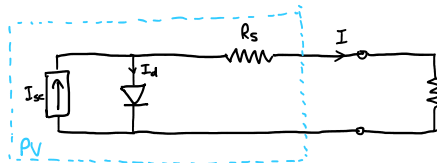
- Add R_s in series to model contact resistance between cells/wires
- Updated PV model with R_s




$$I = I_{sc} - I_d$$

$$I = I_{sc} - I_0 \left(e^{\frac{qV}{kT}} - 1 \right)$$

$$V_d = V + IR_s$$

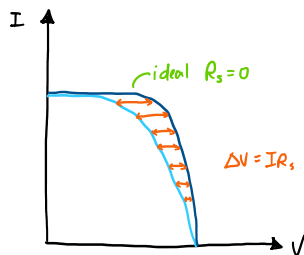

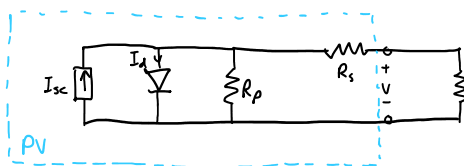- Updated equivalent circuit model with R_p and R_s



$$I = I_{sc} - I_d - \frac{V_d}{R_p}$$

$$= I_{sc} - I_0 \left(e^{\frac{qV_d}{kT}} - 1 \right) - \frac{V_d}{R_p}$$


$$V_d = V + IR_s$$

$$I = I_{sc} - I_0 \left(e^{\frac{q(V+IR_s)}{kT}} - 1 \right) - \frac{V+IR_s}{R_p}$$

> Complicated! No explicit solution for V or I


Maximum Power Point

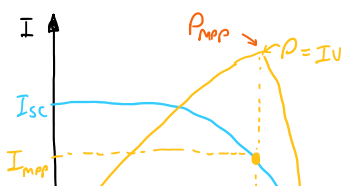Important Characteristics : 1) I_{sc} 2) V_{oc} 3) P_{mpp}



$$\boxed{\text{Fill Factor}} = \frac{P_{mpp}}{V_{oc} I_{sc}}$$

Best Commercial Cell: $FF \cong 0.7$

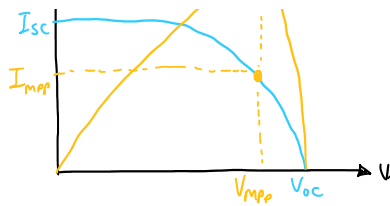


Best Commercial Cell: $FF \cong 0.7$



Best Commercial Cell: $FF \cong 0.7$

• Factors that affect I-V curve

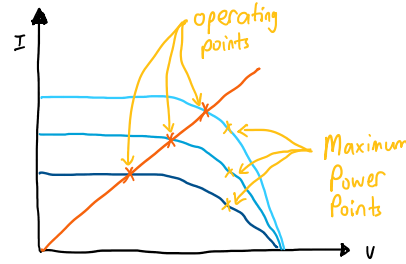- 1) Solar Irradiance
- 2) Temperature
- 3) Shading




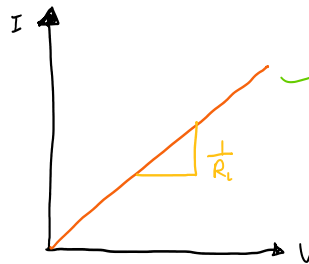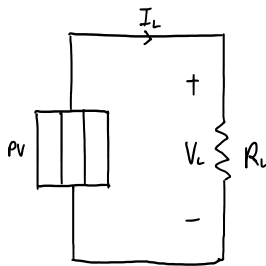Q What if we just connect a load R_L at the output?



> R_L is fixed, but in general $(V_L, I_L) \neq (V_{mpp}, I_{mpp})$

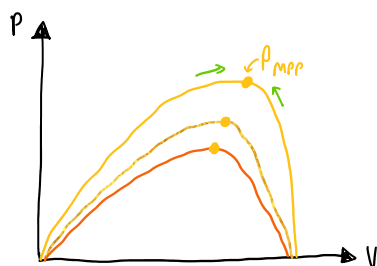
- ↳ don't want to connect PV directly to load
- ↳ want a circuit between PV and load
- ↳ "track" MPP



MPPT Controllers

- dozens of methods/algorithms
- e.g. Perturb & Observe
 - simple, okay for ideal case
 - oscillate around max power

• e.g. Incremental Conductance Model

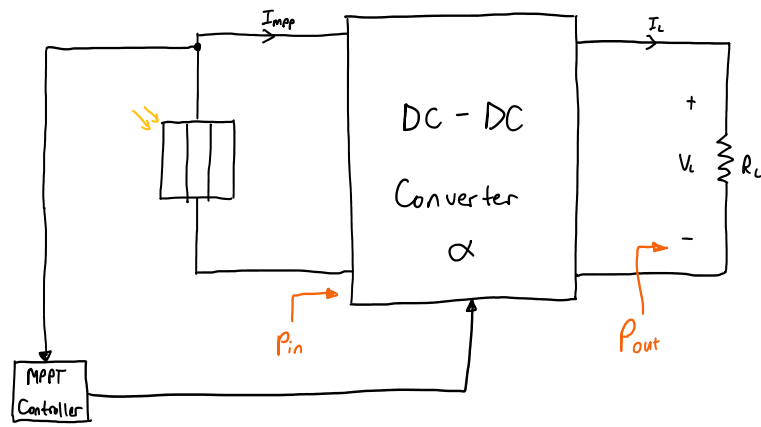

$$V_L = \alpha V_{mpp}$$

$$P_{in} = P_{out}$$

$$V_L I_L = V_{mpp} I_{mpp}$$

$$\rightarrow I_L = \frac{1}{\alpha} I_{mpp}$$